

Logic Circuits

Chapter 3.5

This Chapter:

- 1) Using Boolean algebra with logic gates
- 2) Techniques to simplify circuits
- 3) Karnaugh maps

Data representation

Chapter 3.5 is about how Boolean algebra relates to computer circuits.

This is based on how computers store data as binary - 0's and 1's. This is true for representation of letters and numbers, as well as representing different kinds of commands that a computer can run.

Data representation

Perhaps you've seen an ASCII table at some time:

ASCII TABLE

Decimal	Hex	Char	Decimal	Hex	Char	Decimal	Hex	Char	Decimal	Hex	Char
0	0	[NULL]	32	20	[SPACE]	64	40	@	96	60	`
1	1	[START OF HEADING]	33	21	!	65	41	A	97	61	a
2	2	[START OF TEXT]	34	22	"	66	42	B	98	62	b
3	3	[END OF TEXT]	35	23	#	67	43	C	99	63	c
4	4	[END OF TRANSMISSION]	36	24	\$	68	44	D	100	64	d
5	5	[ENQUIRY]	37	25	%	69	45	E	101	65	e
6	6	[ACKNOWLEDGE]	38	26	&	70	46	F	102	66	f
7	7	[BELL]	39	27	'	71	47	G	103	67	g
8	8	[BACKSPACE]	40	28	(72	48	H	104	68	h
9	9	[HORIZONTAL TAB]	41	29)	73	49	I	105	69	i
10	A	[LINE FEED]	42	2A	*	74	4A	J	106	6A	j
11	B	[VERTICAL TAB]	43	2B	+	75	4B	K	107	6B	k
12	C	[FORM FEED]	44	2C	,	76	4C	L	108	6C	l
13	D	[CARRIAGE RETURN]	45	2D	-	77	4D	M	109	6D	m
14	E	[SHIFT OUT]	46	2E	.	78	4E	N	110	6E	n
15	F	[SHIFT IN]	47	2F	/	79	4F	O	111	6F	o
16	10	[DATA LINK ESCAPE]	48	30	0	80	50	P	112	70	p
17	11	[DEVICE CONTROL 1]	49	31	1	81	51	Q	113	71	q
18	12	[DEVICE CONTROL 2]	50	32	2	82	52	R	114	72	r
19	13	[DEVICE CONTROL 3]	51	33	3	83	53	S	115	73	s
20	14	[DEVICE CONTROL 4]	52	34	4	84	54	T	116	74	t
21	15	[NEGATIVE ACKNOWLEDGE]	53	35	5	85	55	U	117	75	u
22	16	[SYNCHRONOUS IDLE]	54	36	6	86	56	V	118	76	v
23	17	[ENG OF TRANS. BLOCK]	55	37	7	87	57	W	119	77	w
24	18	[CANCEL]	56	38	8	88	58	X	120	78	x
25	19	[END OF MEDIUM]	57	39	9	89	59	Y	121	79	y
26	1A	[SUBSTITUTE]	58	3A	:	90	5A	Z	122	7A	z
27	1B	[ESCAPE]	59	3B	;	91	5B	[123	7B	{
28	1C	[FILE SEPARATOR]	60	3C	<	92	5C	\	124	7C	
29	1D	[GROUP SEPARATOR]	61	3D	=	93	5D]	125	7D	}
30	1E	[RECORD SEPARATOR]	62	3E	>	94	5E	^	126	7E	~
31	1F	[UNIT SEPARATOR]	63	3F	?	95	5F	_	127	7F	[DEL]

From <https://commons.wikimedia.org/wiki/File:ASCII-Table-wide.svg>

Data representation

Perhaps you've seen an ASCII table at some time:

ASCII TABLE

Decimal	Hex	Char	Decimal	Hex	Char	Decimal	Hex	Char	Decimal	Hex	Char
0	0	[NULL]	32	20	[SPACE]	64	40	@	96	60	`
1	1	[START OF HEADING]	33	21	!	65	41	A	97	61	a
2	2	[START OF TEXT]	34	22	"	66	42	B	98	62	b
3	3	[END OF TEXT]	35	23	#	67	43	C	99		
4	4	[END OF TRANSMISSION]	36	24	\$	68	44	D	100		
5	5	[ENQUIRY]	37	25	%	69	45	E	101		
6	6	[ACKNOWLEDGE]	38	26	&	70	46	F	102	66	f
7	7	[BELL]	39	27	'	71	47	G	103	67	g
8	8	[BACKSPACE]	40	28	(72	48	H	104	68	h
9	9	[HORIZONTAL TAB]	41	29)	73	49	I	105	69	i
10	A	[LINE FEED]	42	2A	*	74	4A	J	106	6A	j
11			43	2B	+	75	4B	K	107	6B	k
12			44	2C	,	76	4C	L	108	6C	l
13			45	2D	-	77	4D	M	109	6D	m
14	E	[SHIFT OUT]	46	2E	.	78	4E	N	110	6E	n
15	F	[SHIFT IN]	47	2F	/	79	4F	O	111	6F	o
16	10	[DATA LINK ESCAPE]	48	30	0	80	50	P	112	70	p
17	11	[DEVICE CONTROL 1]	49	31	1	81	51	Q	113	71	q
18	12	[DEVICE CONTROL 2]	50	32	2	82					
19	13	[DEVICE CONTROL 3]	51	33	3	83					
20	14	[DEVICE CONTROL 4]	52	34	4	84					
21	15	[NEGATIVE ACKNOWLEDGE]	53	35	5	85					
22	16	[SYNCHRONOUS IDLE]	54	36	6	86					
23	17	[ENG OF TRANS. BLOCK]	55	37	7	87					
24	18	[CANCEL]	56	38	8	88					
25	19	[END OF MEDIUM]	57	39	9	89	59	Y	121	79	y
26	1A	[SUBSTITUTE]	58	3A	:	90	5A	Z	122	7A	z
27	1B	[ESCAPE]	59	3B	;	91	5B	[123	7B	{
28	1C	[FILE SEPARATOR]	60	3C	<	92	5C	\	124	7C	
29	1D	[GROUP SEPARATOR]	61	3D	=	93	5D]	125	7D	}
30	1E	[RECORD SEPARATOR]	62	3E	>	94	5E	^	126	7E	~
31	1F	[UNIT SEPARATOR]	63	3F	?	95	5F	_	127	7F	[DEL]

'A' = 65

Backspace = 9

'a' = 97

Notice that numbers are given as codes for letters, numbers, and even computer commands that don't have a graphical representation have codes.

These number codes are further translated into binary somewhere along the line.
'A' is 65, and in binary it is 0100 0001.

From <https://commons.wikimedia.org/wiki/File:ASCII-Table-wide.svg>

Data representation

Once we get into the Assembly level, the lowest level programming we can do (except for programming directly in binary), our binary representations look like this:

Addition
Bitfields:

MIPS Assembly code: `ADD rd, rs, rt`

000000	rs	rt	rd	00000	100000
--------	----	----	----	-------	--------

Subtraction
Bitfields:

MIPS Assembly code: `SUB rd, rs, rt`

000000	rs	rt	rd	00000	100010
--------	----	----	----	-------	--------

Branch if equal
Bitfields:

MIPS Assembly code: `BEQ rs,rt,offset`

000100	rs	rt	offset
--------	----	----	--------

Data representation

**So when you write Assembly code,
it has a 1:1 translation to binary.
And with higher-level languages, one command may
translate to several Assembly commands.**

main:

load values into "temp" registers

li \$t0, 2 # \$t0 = 2

li \$t1, 5 # \$t1 = 5

add unsigned integers

addu \$s0, \$t0, \$t1 # \$s0 = \$t0 + \$t1

display value of \$s0

li \$v0, 1 # prepare to output number


move \$a0, \$s0 # load parameter

syscall # display

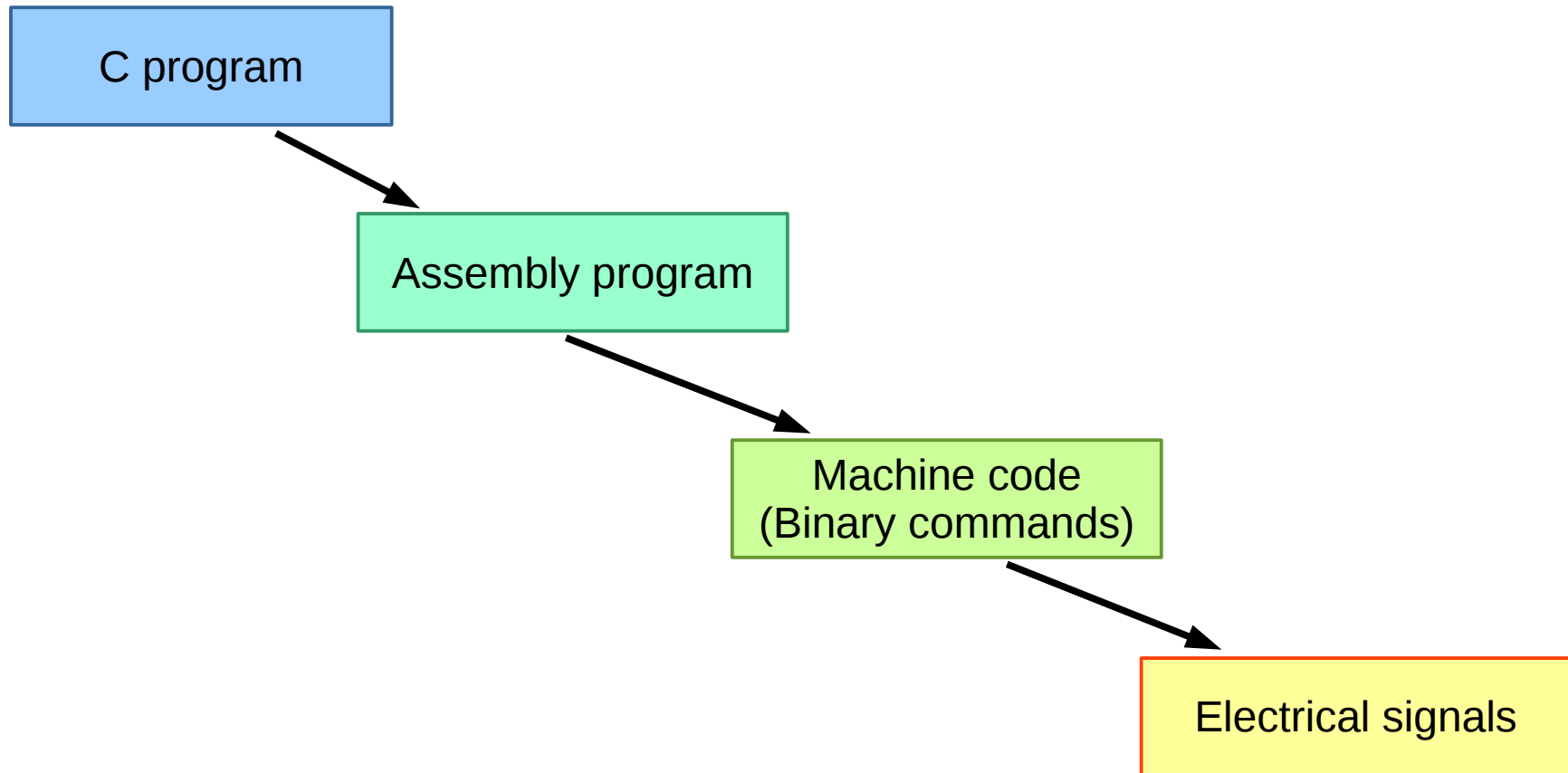**Example MIPS
assembly code**

Data representation

So everything ends up boiling down to *binary* electric signals...








Logic Gates

Logic gates

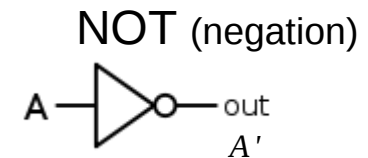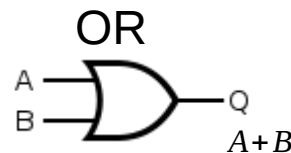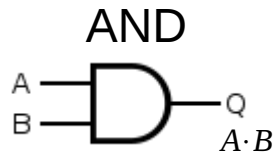When designing circuits, some of the tools we have are logic gates to handle and, or, and not.



Gate images:

https://en.wikipedia.org/wiki/AND_gate , https://en.wikipedia.org/wiki/OR_gate

[https://en.wikipedia.org/wiki/Inverter_\(logic_gate\)](https://en.wikipedia.org/wiki/Inverter_(logic_gate))

Logic gates

Using truth tables, we can see the results of
 $A \cdot B$, $A + B$, and A'
for some given inputs.


Now we use 0 and 1 instead of "T" and "F".

AND




A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

OR

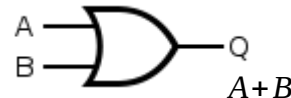

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

NOT (negation)

 

A	A'
0	1
1	0


Gate images:

https://en.wikipedia.org/wiki/AND_gate , https://en.wikipedia.org/wiki/OR_gate

[https://en.wikipedia.org/wiki/Inverter_\(logic_gate\)](https://en.wikipedia.org/wiki/Inverter_(logic_gate))

Logic gates

 
Example: Consider the following diagram. What is the Boolean algebra equation, and the truth table?



What does this final result symbolize?

Logic gates

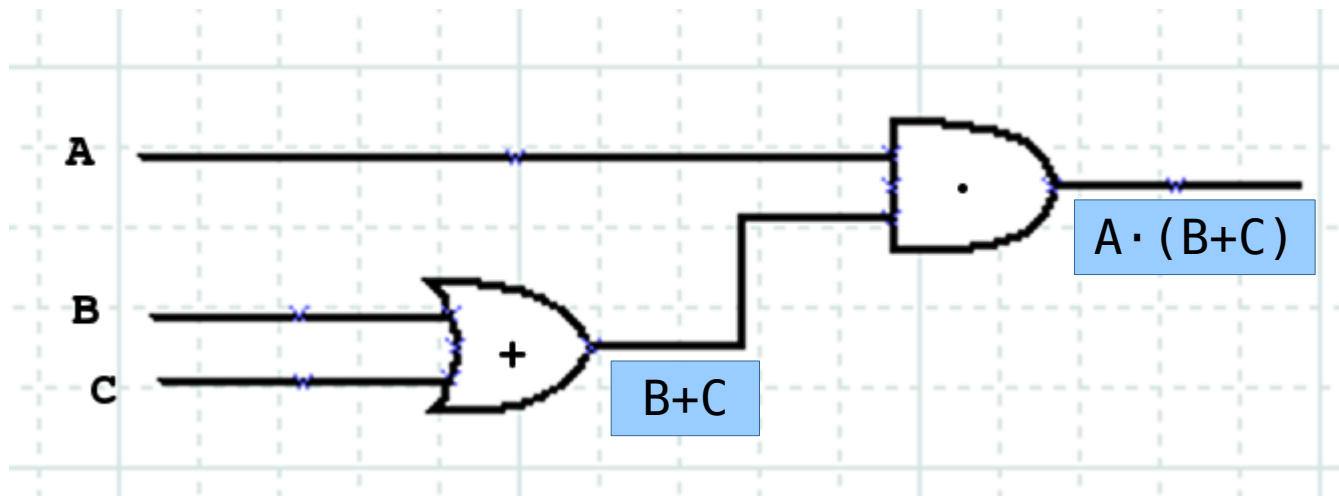
Example: Consider the following diagram. What is the Boolean algebra equation, and the truth table?



And what is the truth table for this diagram?

Logic gates

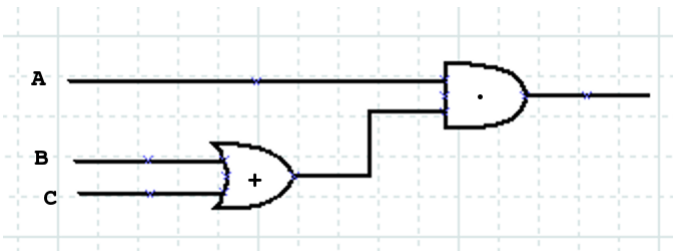Example: Consider the following diagram. What is the Boolean algebra equation, and the truth table?



A	B	C	$B+C$	$A \cdot (B+C)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Boolean algebra properties

Just like with our logic and set properties, we also have similar properties for Boolean algebra:

(a) Commutative: $a \cdot b = b \cdot a$ $a + b = b + a$

(b) Distributive:
 $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
 $a + (b \cdot c) = (a + b) \cdot (a + c)$

(c) Identity: $a \cdot 1 = a$ $a + 0 = a$

(d) Negation: $a + a' = 1$ $a \cdot a' = 0$

Boolean algebra properties

Just like with our logic and set properties, we also have similar properties for Boolean algebra:

(a) Commutative: $a \cdot b = b \cdot a$ $a + b = b + a$

So it is possible for two gate diagrams to be **logically equivalent**, even if they're designed differently.

(b) Distributive: $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$

Think of how this might affect the design of the physical hardware – we want the simplest design to save space and components.

(c) Identity: $a \cdot 1 = a$ $a + 0 = a$

(d) Negation: $a + a' = 1$ $a \cdot a' = 0$

Practice

Example 2 from the textbook

Show that

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

with a truth table...

Practice

Example 2 from the textbook

Show that

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

with a truth table...


a	b	c	$b \cdot c$	$a + b \cdot c$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

a	b	c	$a + b$	$a + c$	$(a + b) \cdot (a + c)$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

Practice


Practice problem 2 from the textbook

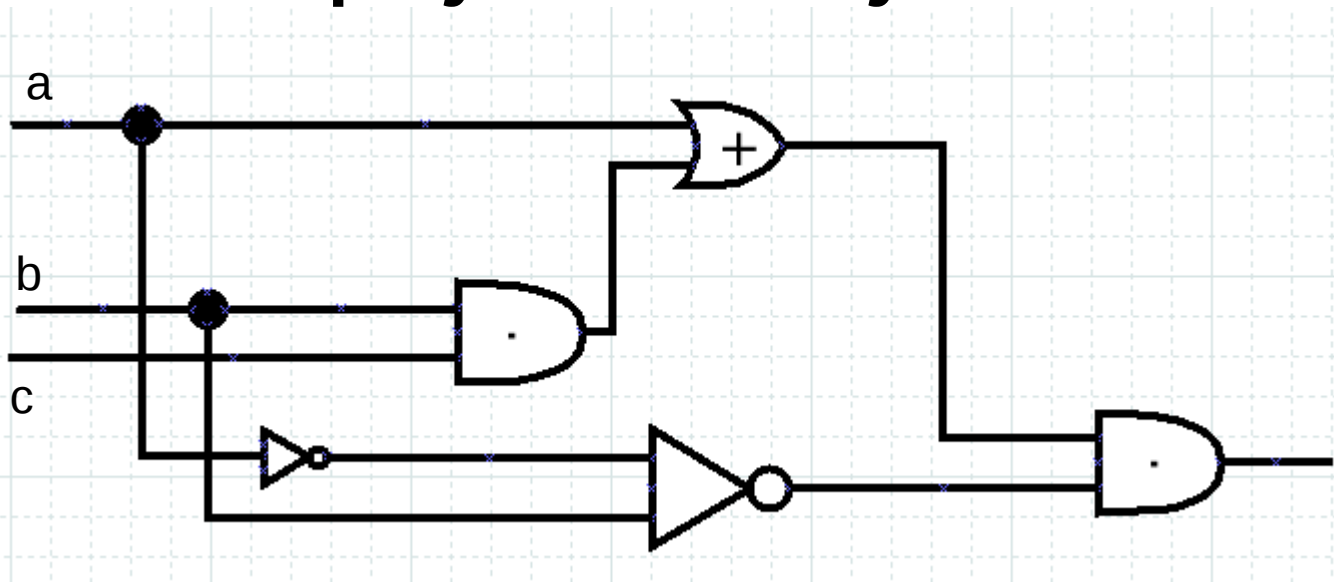**Write the Boolean expression for the circuit diagram,
and simplify as much as you can.**



Practice

 Practice problem 2 from the textbook
Write the Boolean expression for the circuit diagram,
and simplify as much as you can.



$$\begin{aligned} & (a + bc)(a'b)' \\ = & (a + bc)(a + b') \\ = & (a + (bc)b') \\ = & a + cbb' \\ = & a + c0 \\ = & a + 0 \\ = & a \end{aligned}$$



Karnaugh Maps

K-maps: Two variables

Karnaugh maps are used to simplify boolean expressions. Instead of using a truth table, we draw our expression in a grid. We display all possible terms, and simplify.

	y	y'
x		
x'		

K-maps: Two variables

Example: Let's look at $xy + xy'$

If we look at it, we can see that it says "x and y, or x and not y", which we can logically reduce on our own, but let's use a map.

K-maps: Two variables

Example: Let's look at $xy + xy'$

First, we mark the two products on our grid.

	y	y'
x	✓	✓
x'		

K-maps: Two variables

Example: Let's look at $xy + xy'$

First, we mark the two products on our grid.

Then we draw a rectangle around adjacent blocks that have been ✓ d off.

Rectangles are what represent where we can simplify.

	y	y'
x	✓	✓
x'		

K-maps: Two variables

Example: Let's look at $xy + xy' = x$

The rectangle contains all states in the “x” row, so the simplified version here is just x .

If we had multiple rectangles, then our simplified form would be the sum of these rectangles.

	y	y'
x	✓	✓
x'		

K-maps: Two variables

Example: Let's look at $xy + xy' = x$

We can also verify this mathematically:

$$\begin{aligned} & xy + xy' \\ = & x(y + y') && y + y' = 1 \\ = & x \cdot 1 \\ = & x \end{aligned}$$

	y	y'
x	✓	✓
x'		

Practice

Example 6 from book: Simplify $xy' + x'y'$ with a Karnaugh map.

	y	y'
x		
x'		

Practice

Example 6 from book: Simplify $xy + xy' + x'y$ with a Karnaugh map.


1. Place checkmarks

	y	y'
x	✓	✓
x'	✓	

Practice

Example 6 from book: Simplify $xy + xy' + x'y$ with a Karnaugh map.

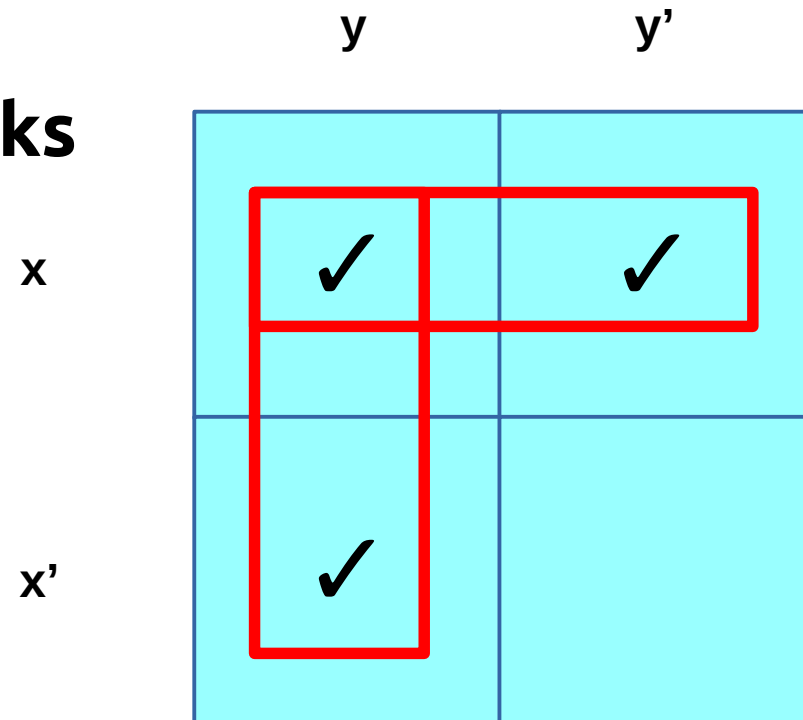- 1. Place checkmarks**
- 2. Region off adjacent checks**




Practice

Example 6 from book: Simplify $xy + xy' + x'y$ with a Karnaugh map.

- 1. Place checkmarks**
- 2. Region off adjacent checks**
- 3. Result is the sum of these regions (based on row/col that is filled in)**

$$x + y$$

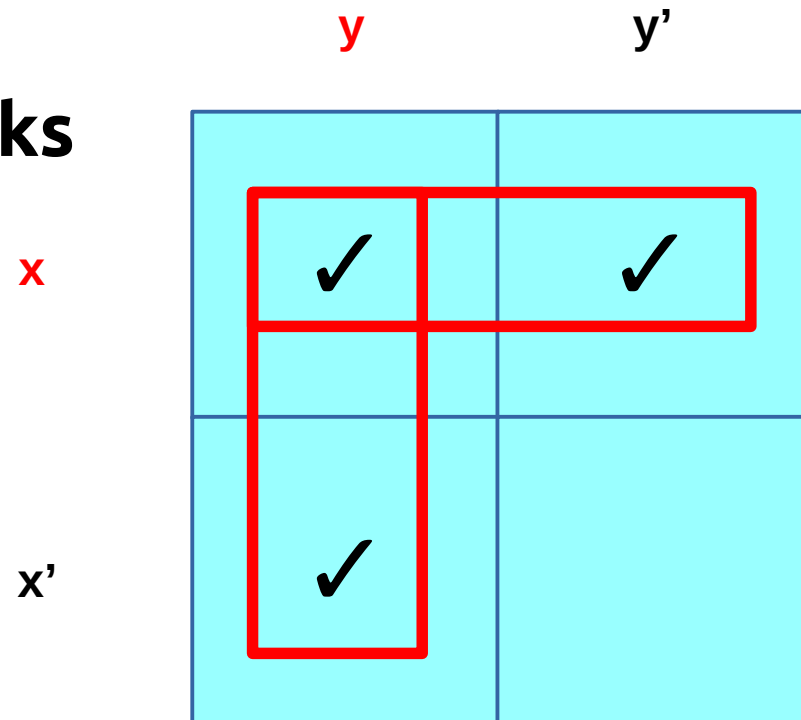

No simplification

Sometimes when you build a map, there is just no simplification, such as with this grid.

There are no adjacent blocks with ✓ marks, so it cannot be simplified.

	y	y'
x		✓
x'	✓	

K-maps: Three variables

What about when we have three variables? Then we build our Karnaugh map grid as it is below.

For the columns, labels in each column that are next to each other differ by only one variable – in other words, you can't go from yz to $y'z'$ in neighbors.

	yz	yz'	$y'z'$	$y'z$
x				
x'				

Simplification guidelines

There are also additional guidelines for us to find the simplest expression with a Karnaugh map. There are different ways to find rectangles, but they're not necessarily the most simplified forms.

	yz	yz'	$y'z'$	$y'z$
x		✓	✓	
x'		✓	✓	

	yz	yz'	$y'z'$	$y'z$
x		✓	✓	
x'		✓	✓	

	yz	yz'	$y'z'$	$y'z$
x		✓	✓	
x'		✓	✓	


Wrapping around

For these maps, our rectangles can also **WRAP AROUND**.

	yz	yz'	$y'z'$	$y'z$
x				
x'	✓			✓

Wrapping around

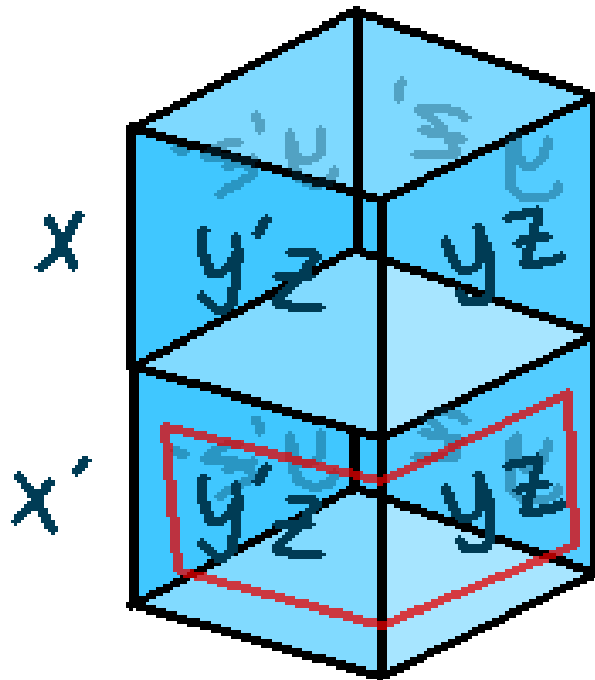yz and $y'z$ are only one tiny difference apart, so perhaps it might be useful to think of the map as a 3D shape instead, which keeps looping.



	yz	yz'	$y'z'$	$y'z$
x				
x'	✓			✓

Smallest # of rectangles

Choose rectangles in a way that yields the smallest number of total rectangles, and that each rectangle is as large as possible.

	yz	yz'	$y'z'$	$y'z$
x		✓	✓	✓
x'		✓	✓	

Size 3 not allowed

Lengths of size 3 are not allowed: only length 1, 2, or 4.

(If it were size 3, you wouldn't have full coverage of a row. 1 is allowed because it would be anything left over.)

	yz	yz'	$y'z'$	$y'z$
x		✓	✓	✓
x'		✓	✓	

Missing variables

If the equation has a term without one of the variables, then realize that the expression is true for both “true” and “false” for that missing variable.

xy means xyz and xyz' .

	yz	yz'	$y'z'$	$y'z$
x	✓	✓		
x'				

Karnaugh map for xy

Examples

Examples

$$xyz + xyz' + xy'z' + xy'z = x$$

The full row for x is filled in with \checkmark marks, meaning that x is the only variable that actually affects the outcome of the equation.

	yz	yz'	$y'z'$	$y'z$
x	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
x'	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Examples

Examples

$$xyz' + xy'z' + x'yz' + xy'z' = z'$$

Notice that the two columns that are “full” are the ones that belong to z' .

z' is always present, whether we have x , x' , y , or y' .

	yz	yz'	$y'z'$	$y'z$
x		✓	✓	
x'		✓	✓	

Practice

Example 9 from the book: Simplify

$$xyz + xy'z' + xy'z + x'yz + x'y'z$$

to the simplest form.

	yz	yz'	$y'z'$	$y'z$
x	✓		✓	✓
x'	✓			✓

Practice

Example 9 from the book: Simplify

$$xyz + xy'z' + xy'z + x'yz + x'y'z$$

to the simplest form.

Here's the map...

	yz	yz'	y'z'	y'z
x	✓		✓	✓
x'	✓			✓

Practice

Example 9 from the book: Simplify

$$xyz + xy'z' + xy'z + x'yz + x'y'z$$

to the simplest form.

Here's the map...

Result is

$$z + xy'$$


	yz	yz'	y'z'	y'z
x	✓		✓	✓
x'	✓			✓

K-maps: Four variables


“Are we done yet?!”

Not yet... we can also work with maps of four variables.

“...dang.”

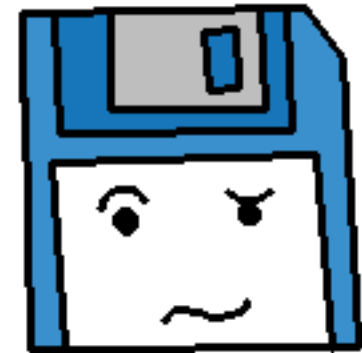

K-maps: Four variables

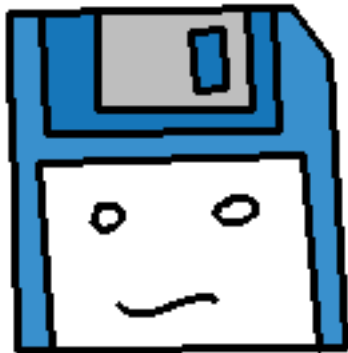

	zw	zw'	$z'w'$	$z'w$
xy				
xy'				
$x'y'$				
$x'y$				

K-maps: Four variables

Aren't you exited?

Well, anyway...

	zw	zw'	$z'w'$	$z'w$
xy				
xy'				
$x'y'$				
$x'y$				

K-maps: Four variables

Keep in mind with these maps, now for columns and rows both, labels that are next to each other differ only by one.

And again, we can have wrap-around, but this time in both directions.

	zw	zw'	z'w'	z'w
xy				
xy'				
x'y'				
x'y				

K-maps: Four variables

Example 10 from the book: Simplify

$$xyz'w' + xy'z'w' + xy'z'w + x'y'z'w' + x'yz'w'$$

	zw	zw'	z'w'	z'w
xy				
xy'				
x'y'				
x'y				

K-maps: Four variables

Example 10 from the book: Simplify

$$xyz'w' + xy'z'w' + xy'z'w + x'y'z'w' + x'yz'w'$$

Map...

	zw	zw'	z'w'	z'w
xy			✓	
xy'			✓	✓
x'y'			✓	
x'y			✓	

K-maps: Four variables

Example 10 from the book: Simplify

$$xyz'w' + xy'z'w' + xy'z'w + x'y'z'w' + x'yz'w'$$

Map...

Regions...

	zw	zw'	z'w'	z'w
xy			✓	
xy'			✓	✓
x'y'			✓	
x'y			✓	

K-maps: Four variables

Example 10 from the book: Simplify

$$xyz'w' + xy'z'w' + xy'z'w + x'y'z'w' + x'yz'w'$$

Map...

Regions...

$$= xy'z' +$$

	zw	zw'	z'w'	z'w
xy			✓	
xy'			✓	✓
x'y'			✓	
x'y			✓	

K-maps: Four variables

Example 10 from the book: Simplify

$$xyz'w' + xy'z'w' + xy'z'w + x'y'z'w' + x'yz'w'$$

Map...

Regions...

$$= xy'z' + z'w'$$

	zw	zw'	z'w'	z'w
xy			✓	
xy'			✓	✓
x'y'			✓	
x'y			✓	

K-maps: Four variables

Example 10 from the book: Simplify

$$xyz'w' + xy'z'w' + xy'z'w + x'y'z'w' + x'yz'w'$$

Map...

Regions...

$$= xy'z' + z'w'$$

Got it?

	zw	zw'	z'w'	z'w
xy			✓	
xy'			✓	✓
x'y'			✓	
x'y			✓	

Practice


Example 12 from the book: Build the simplest regions for this map.

	zw	zw'	$z'w'$	$z'w$
xy	✓			✓
xy'	✓	✓		
$x'y'$				
$x'y$	✓			✓

Practice

 Example 12 from the book: Build the simplest regions for this map.

Don't forget
about being
able to wrap
around in all
directions!



Practice

Example 13 from the book: Simplify
 $y'w' + yz + x'yw'$

	zw	zw'	z'w'	z'w
xy				
xy'				
x'y'				
x'y				

Practice

Example 13 from the book: Simplify
 $y'w' + yz + x'yw'$

Remember that when variables are missing, we add them in as both the normal and prime forms.

$y'w' =$
 $(xz)y'w' \text{ or } (x'z)y'w'$
or $(x'z')y'w' \text{ or } (xz')y'w' \dots$

	zw	zw'	z'w'	z'w
xy	✓	✓		
xy'		✓	✓	
x'y'		✓	✓	
x'y	✓	✓	✓	

Practice

Example 13 from the book: Simplify
 $y'w' + yz + x'yw'$

So the simplest form is


$$y'w' + yz + x'w'$$

(tried to use circles to make it easier to see the overlapped regions)

A 4x4 Karnaugh map for variables x, y, z, w. The columns are labeled zw, zw', z'w', and z'w. The rows are labeled xy, xy', x'y', and x'y. The map contains checkmarks in the following cells: (xy, zw), (xy, zw'), (xy', zw'), (xy', z'w'), (x'y', zw'), (x'y', z'w'), (x'y, zw), (x'y, zw'), and (x'y, z'w). Three red circles highlight overlapping groups: one circle around the top-left two cells (xy, zw) and (xy, zw'); another circle around the middle two cells (xy', zw') and (xy', z'w'); and a third circle around the bottom two cells (x'y, zw) and (x'y, zw').

	zw	zw'	z'w'	z'w
xy	✓	✓		
xy'		✓	✓	
x'y'		✓	✓	
x'y	✓	✓	✓	

Alright, we're done now.

 

	y	y'
x		✓
x'	✓	✓

	yz	yz'	$y'z'$	$y'z$
x				
x'				